

VK5TM Noise Canceller

(Updated August 2020)

See website for pcb & kit availability and latest up to date information. Website URL's in blue italic text are clickable.

<http://www.vk5tm.com/homebrew/noisecancel/noisecancel.php>

ERRATA - In the SPRAT magazine article, there is a cap (C16) missing from the circuit diagram. The circuit diagram on this page is up to date.

*****LF/MF Mod - see bottom of page*****

The original version of the Noise Canceller, as far as I can tell, was developed about 1989 by G4WMX and GW3DIX. A similar device was also available commercially from SEM as the QRM Eliminator. Later, Hans DK9NL updated it to include a HF Vox circuit. Klaus DG0KW made further refinements and it was published in Funkamateure in 2013.

The VK5TM Noise Canceller is another version of the design, with the HF Vox circuit removed (it proved unreliable on SSB transmission) and a couple of other minor changes, including the use of SMD JFETs and a double-sided pcb.

The operation of the circuit involves the cancellation of local interfering signals, that are picked up on a relatively inefficient 'noise antenna' and are made 180 degrees out of phase with the signal on the main antenna, which also contains the interfering signal plus the wanted signal. After the mixing of the two interfering signals, the main wanted signal remains. Tony G4WIF's blog at <http://www.fishpool.org.uk/noisecancel.htm> has a nice list of links (supplied by Nick G8INE) to further information.

It should be pointed out that this circuit is not a cure for broadband, multiple noise sources. If you are experiencing this sort of interference, you should probably be looking more towards DSP noise cancelling techniques.

Several points should be noted:-

Without power applied the circuit is in bypass mode (so you shouldn't do any damage transmitting into an unpowered unit), but transmitting into a powered unit without the PTT connected will damage the electronics.


Maximum transmit power through this unit should be 100w or less.

The changeover relays are two 6V 3A contact rated units wired in series. A 220uF capacitor in series with the supply enables quick operation of the relays, while the paralleled 150 Ohm resistor reduces the hold current once the capacitor has charged.

The bandwidth of the unit is determined by transformer T1, depending on the core used and number of windings. This is an area you can experiment with.

There is nothing out of the ordinary as regards the circuit and construction is straight forward.

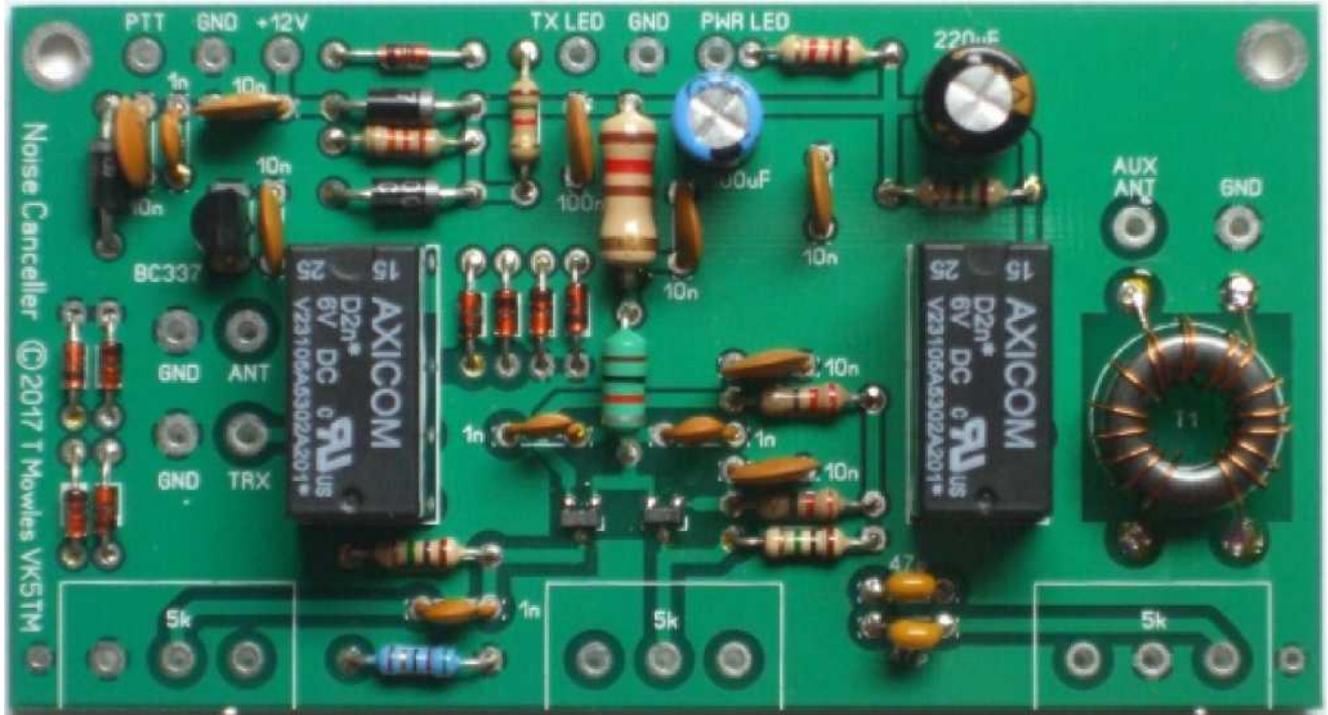
Relays 1 & 2 can be fitted next followed by transformer T1, see below for receive only option. T1 is 16 turns secondary/4 turns primary, 0.3-0.4mm enamelled copper wire, wound on an FT50-43 toroid core (0.5mm wire was used in the prototype and is supplied in the kit, it is somewhat easier to handle).



Winding the toroid

Me and my fat fingers are not the best at winding toroids, but here is one way of doing it and making sure the primary winding is centered on the secondary winding. You will probably have your own favourite method, including throwing it out the window when it gets really annoying. For the secondary you will need approximately 350mm of wire and 130mm of wire for the primary.

Fold each piece in half.

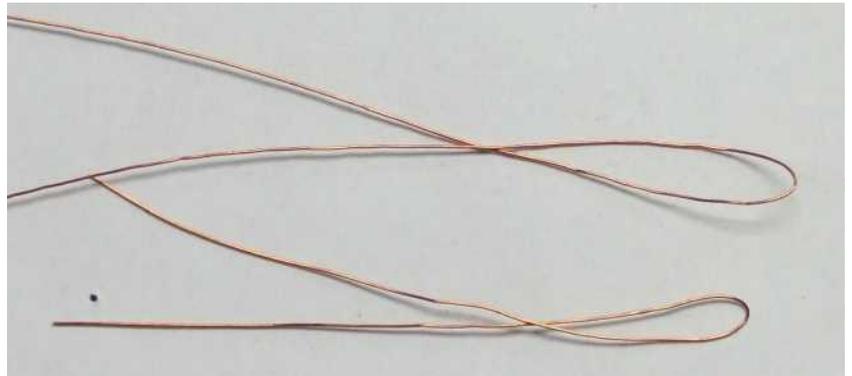


Then, keeping the wires together, twist them together. Don't worry about how many "turns to the inch" or whatever, it's only a short length and won't make a great deal of difference.




Now place the wire so one leg goes through the central hole and wind 4 turns symmetrically from that point (remember - once through the hole = 1 turn).

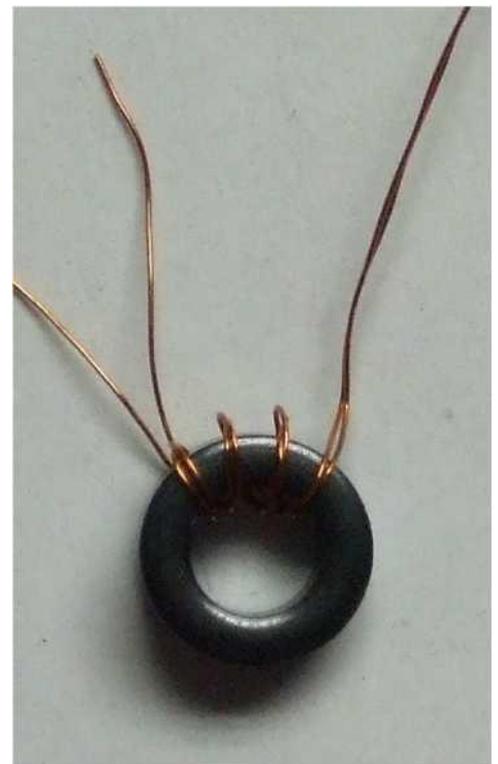Unwind the remaining length of the short wire from the longer length.



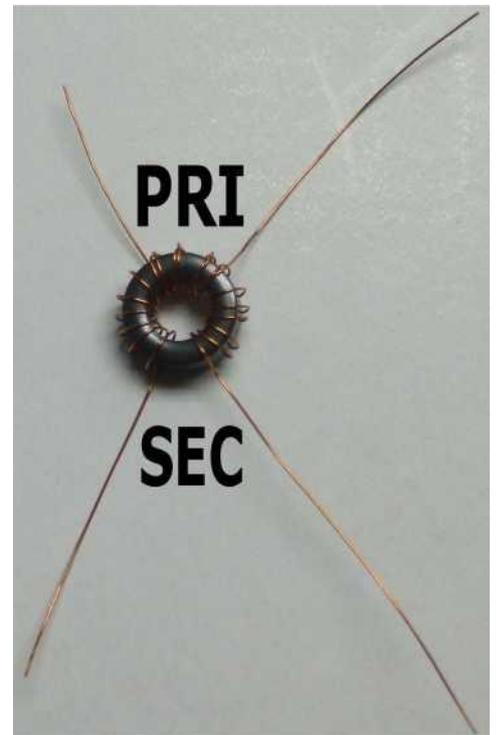All that remains is to curse your not so nimble fingers and wind the remaining wire onto the toroid for a total of 16 turns.




If you are going to use this unit "portable", ie out in the field, I would strongly recommend securing the toroid to the pcb. Either by gluing it down or drilling a hole in the center and using a nylon (or similar) nut, bolt, washer combination - **DO NOT USE A METAL NUT, BOLT OR WASHER.**

Construction continued...

Finally, fit the three potentiometers. An earth wire is then soldered from the earth point on one side of the potentiometers, across the top of the potentiometers to the earth point at the other side. This wire is then soldered to the body of each of the potentiometers.

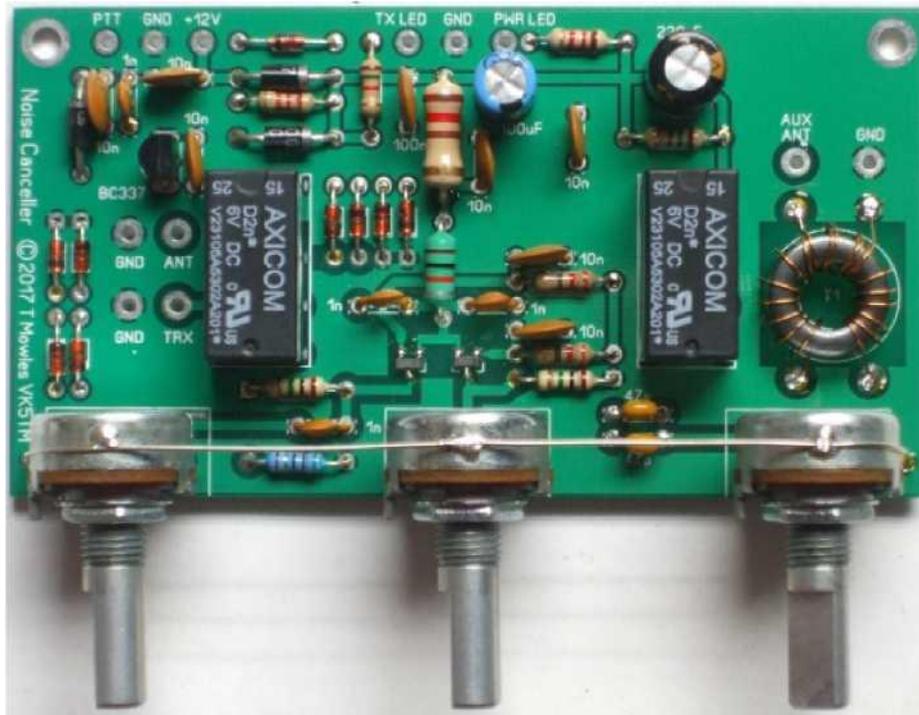
Hand capacitance has a marked effect on the controls, particularly VR2 (Phase 2), as does stray external RF, so this unit should be mounted in a metal enclosure. If you have or can source potentiometers with plastic shafts, they would be better than the metal shaft variety, non-metallic knobs should also be used.



Once assembled, double check that all components are correctly oriented.

Receive only option

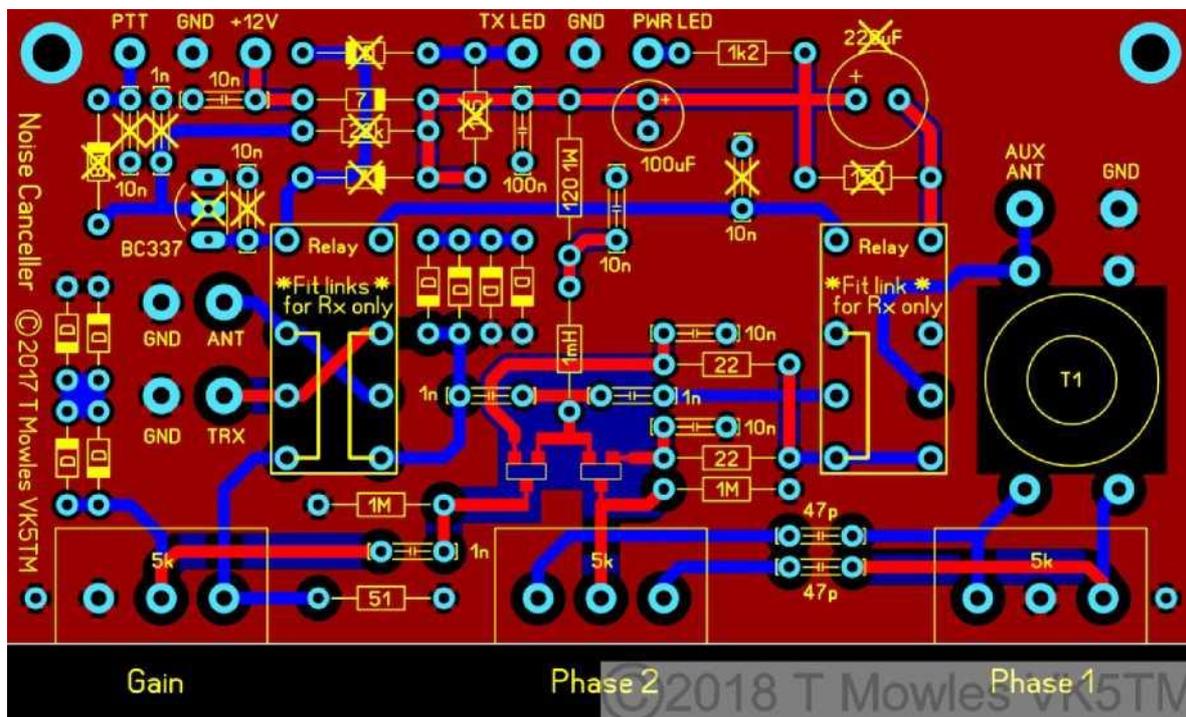If you are building this to use with a Receiver only, you can leave the relays off. You will need to add 3 links in place of the relays as in the overlay below. Additionally, all the components with a cross over them need not be fitted. They are for the PTT/relay control function.



Please make sure you mark somewhere on it that this is for receive only. Transmitting into it will destroy it.

Component substitutes

Diodes have already been mentioned above, which really only leaves the JFETS, BC337 and relays. Firstly the JFETS. If you do decide to substitute something else, **MAKE SURE** the Drain and Source connections are interchangeable, not all JFETS are.

1. Connect a 12-15v power supply (the circuit is diode protected against reverse polarity) and all being well, the power Led should light and the relays click in. If not, disconnect the power and rectify any problems. The current draw at 13.8V, with the relays specified, should be between 90 - 95 mA when the relays are activated and 18 - 20 mA when not activated.
2. If all is OK (and nothing let out the magic smoke), connect the point marked 'PTT' on the pcb to ground and the relays should release and the TX Led come on (note that without power applied, this circuit is automatically in Tx mode). Remove the power.
3. You will need to check with the user manual of your transceiver to see if the PTT output pulls to ground when transmitting. If not, you will need to sort something to make it so, before continuing.

Connect a dummy load to the transceiver (you do have one, don't you?), else connect your station antenna and reduce power on the transceiver to as low as possible.

Connect the 'PTT' line from your transceiver to the point marked 'PTT' on the pcb, you will also need to connect GND of the Noise Canceller to GND of the transceiver.

Do not make any other connections to the Noise Canceller.

Apply power to the Noise Canceller and turn on your transceiver. Push the PTT button and the relays should dropout and the Tx LED should come on.

If all is well, you can turn off both units and proceed to the next steps, otherwise, locate and fix any problems. Second phase of testing.

PLEASE NOTE:- Transmitting into this unit while powered and without the PTT connected and working WILL damage the electronics.

There's two ways to test the rest of the circuit for correct operation, depending on whether you have a 'noise antenna' available yet or not (more about the 'noise antenna' further along).

Option 1 - No noise antenna available yet.

Connect the Noise Canceller 'TRX' connection to the Ant connection of your Transceiver or Receiver (yes, this unit will work on just a Receiver) and connect the PTT line.

Then connect your external antenna to BOTH the 'ANT' and 'AUX ANT' connections (at the same time) of the Noise Canceller. Do not power up the Noise Canceller yet.

Turn on your transceiver and make sure you can still hear signals.

Set all the controls of the Noise Canceller to their mid positions and apply power to the Noise Canceller. Tune in a signal and then adjust all of the controls of the Noise Canceller, starting with the Phase 1 control, for a reduction in the signal. All the controls interact and the null can be quite sharp, but you should be able to remove most, if not all, of the received signal.

Option 2 - With a noise antenna.

OK, basically exactly as in option 1, but connect your main antenna to the 'ANT' connection of the Noise Canceller and your noise antenna to the 'AUX ANT' connection. You will also be looking to cancel any QRM as opposed to a wanted received signal.

If you have an ATU connected to your main antenna, connect the Noise Canceller between the transceiver and ATU and use as normal.

Final Assembly

Once you have completed testing, assemble the Noise Canceller into a metal enclosure, using which ever connectors match what you use in your station for the antenna/rig connections. The connectors for 'PTT' and power can be anything suitable for the purpose.

Reasonable quality RG58 should be used to connect to the RF connectors and it might be an idea to twist together the pairs of wires from the power and PTT connectors and LED's to the pcb.

Noise Antenna

Because everybodies situation is different, it is not possible to say 'you need x type of antenna' in relation to a noise antenna, so these are just some general comments.


Some may get away with just a few turns of wire wrapped around a ferrite rod or a short whip antenna, for others, several feet of wire strung up between two points may be needed.

The one thing you don't want is an efficient antenna as a noise antenna. You need to pick up more of the noise as opposed to the wanted signal, so you will also need to keep the noise antenna away from your main antenna.


Positioning of the noise antenna depends entirely on your own individual situation, so some experimentation as to placement may be needed for the best results, e.g. if you know the QRM is coming from your neighbours plasma tv, place the noise antenna as close as you can to that side. A noise antenna does not need to be 'matched' or 'tuned' to the 'AUX ANT' input.

Connecting Up

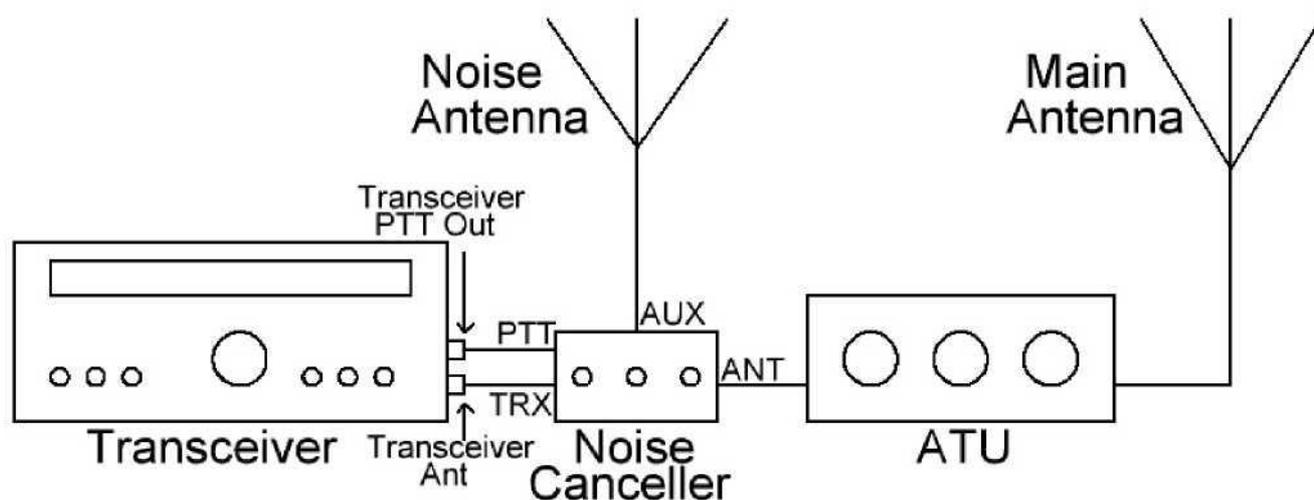Although you have already made the connections in the testing phase, below are a couple of diagrams to make it clearer if necessary.



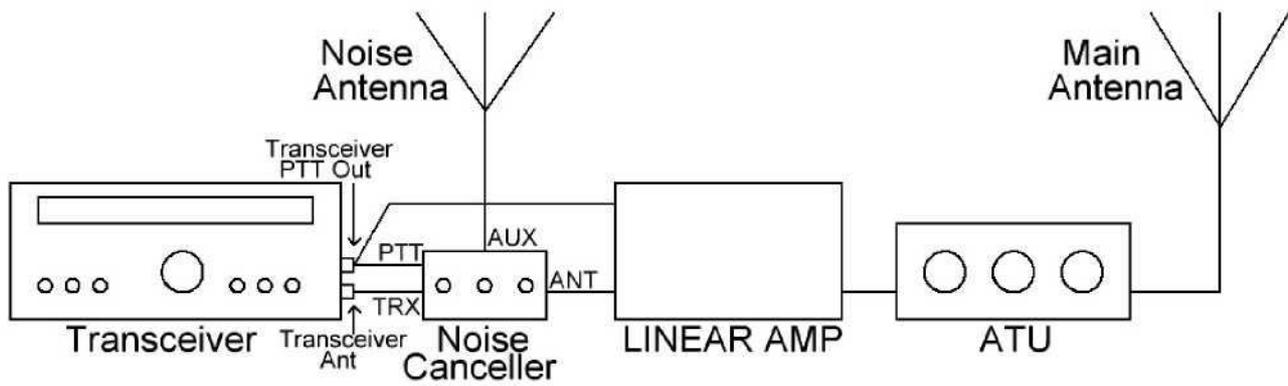If you have a Linear Amp, the Noise Canceller goes between the rig and Linear as below.



LF/MF Mod

I had an email from Max IK0VVE to let me know that he has this Noise Canceller working down at 2200m (136kHz).

He replaced the FT50-43 with a BN73-202. The number of turns used by Max is 8 & 2.

Don't forget that when winding binocular cores, 1 turn is through the hole on one side and back down the hole on the other side. There is a PDF file on the website, hosted by kind permission of Jim Kortge K8IQY and the 4SQRP Group, that shows how to wind a binocular core.

Downloads

See the webpage for this project for the Parts List and any other downloads that may become available. Weblink at the beginning of this document.

© 2020 T Mowles VK5TM. All rights reserved.

VK5TM Noise Canceller Parts List

Updated January 2021 - minor layout revision
See www.vk5tm.com for construction details

Component	QTY	Description
Capacitors		
C1,C6,C7,C9,C13,C15,C16	7	10n ceramic
C2,C3,C4,C14	4	1n ceramic
C5,C8	2	47p ceramic
C10	1	100n ceramic
C11	1	100uF 25v electrolytic
C12	1	220uF 16v electrolytic
Resistors		
All resistors 1/4W except R1 - 1W		
R1	1	120R 1W
R2	1	51R (0.6W supplied in kit)
R3,R6	2	1M
R4,R5	2	22R
R7	1	150R
R8	1	1k5
R9	1	1k2
R10	1	22k
Choke		
L1	1	1mH miniature choke
Diodes		
D1,D2,D3,D4,D5,D6,D7,D8,D12	9	1N4148
D9,D10	2	1N4007
D11	1	BAT85, 1N5819 or similar low forward voltage drop
D13	1	LED Red (3mm supplied in kit)
D14	1	LED Green (3mm supplied in kit)
Transistor/FET		
Q1,Q2	2	MMBFJ310LT3G (J310 smd JFET)
Q3	1	BC 337
Toroid		
T1	1	FT50-43 Toroid
Wire		
	1	500mm x 0.5mm ecw
	1	150mm Tinned copper wire (For earthing Pots)
Relays		
Rel1,2	2	DPDT 6V 3A relay Manufacturer TE Connectivity Part No.V23105A5302A201
Potentiometer		
VR1,VR2,VR3	3	5k Lin 16mm
PCB		
	1	NC01a double-sided pcb